
Example: RLC Series Circuit

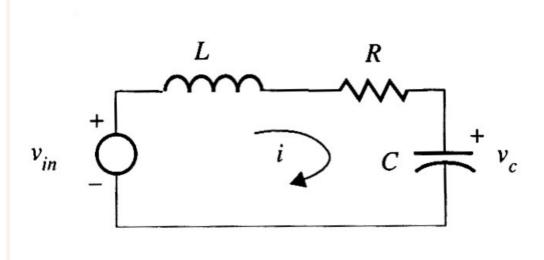

$$v_{in} = input \ voltage \ (volts)$$

L = inductance(H)

 $R = resistance (\Omega)$

 v_c C = capacitance(F)

 $v_c = voltage \ across \ the \ capacitor$

i = current (amps)

Using Kirchhoff's voltage law, we obtain

$$L\frac{di}{dt} + Ri + v_c = v_{in}, (1$$

$$v_c = \frac{1}{C} \int idt.$$

We define the state variables as

$$x_1 = v_c$$

$$x_2 = i$$
.

Then taking the time derivative of x_1 and using Eq. (2) yields

$$\dot{x}_1 = \frac{1}{C} x_2. \tag{3}$$

Also, taking the time derivative of x_2 and using Eq. (1) yields

$$\dot{x}_2 = -\frac{R}{L}x_2 - \frac{1}{L}x_1 + \frac{1}{L}v_{in}.$$
 (4)

We can write Eqs. (3) and (4) in matrix form as

$$\dot{x} = Ax + Bu$$

where
$$x = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} v_c \\ i \end{bmatrix}$$
, $u = v_{in}$,

and
$$A = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix}, B = \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix}.$$

With $R = 10\Omega, L = 0.2H$, and C = 0.0015F, we have

$$\dot{x} = \begin{bmatrix} 0 & 666.6 \\ -5 & -50 \end{bmatrix} x + \begin{bmatrix} 0 \\ 5 \end{bmatrix} u.$$

If we measure v_c , then we have

$$y = Cx + Du$$
,

where
$$C = [1 \ 0], D = [0].$$

$$D = [0].$$

We can also compute the transfer function as

$$\frac{\hat{v}_c(s)}{\hat{v}_{in}(s)} = \hat{G}(s) = C(sI - A)^{-1}B + D.$$

So this case (where we can measure v_c), we have

$$\hat{G}(s) = \frac{1}{LC} \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}.$$

On the other hand, if we can measure i instead of v_c , we have

$$y = Cx + Du,$$

where $C = [0 \ 1], \ and \ D = [0].$

In this case, the transfer function is $\hat{G}(s) = \frac{1}{L} \frac{s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$.

Lab #2 (1 Pt.):

- 1. Write a MATLAB script to simulate the step response of the RLC circuit.
- 2. Plot the time history of the voltage v_c .
- 3. Plot the time history of the current *i*.